
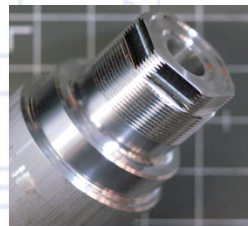
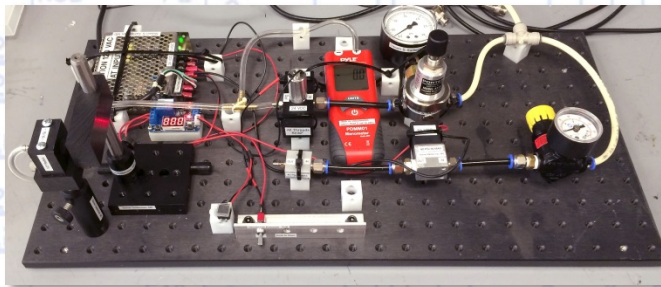
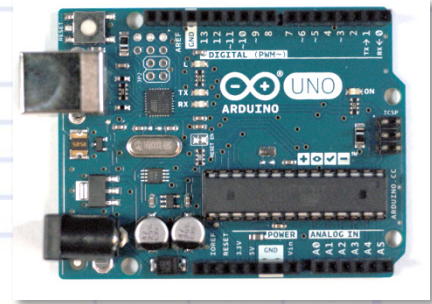
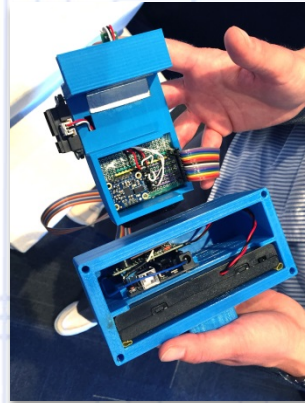


Introductory Medical Device Prototyping

Analog Circuits Part 2 – Semiconductors

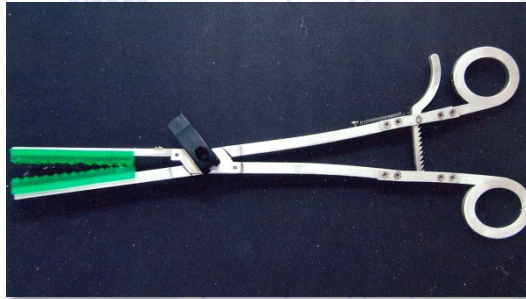Prof. Steven S. Saliterman, <http://saliterman.umn.edu/>
Department of Biomedical Engineering, University of Minnesota



Concepts to be Covered

- Semiconductors
 - Diodes to Rectify Current
 - Zener Diodes for Voltage Reference
 - Voltage Regulators
 - Transistors as Switches
 - Common Emitter Bipolar Junction Transistor Amplifier


Diodes

- Diodes are semiconductor devices that rectify current – allowing flow in only one direction. The larger the current, the larger the diode.
- They may be used as switching devices, voltage-controlled capacitors (varactors) and voltage references (Zener diodes).
- Typically a 2-terminal device – an anode and cathode.
- Ideally resistance is zero in one direction, and infinite in the other.
- Diodes allow current to flow in only one direction and can therefore be used as simple solid state switches in AC circuits, being either open (not conducting) or closed (conducting).
- A bridge rectifier, consisting of 4 diodes can be used to convert AC into DC, and typically followed filtering capacitors and/or Zener diode.





Diode Current to Voltage Relationship



- **Forward bias:** Voltage across the diode is positive and flows.
- **Reverse bias:** This is the “off” mode of the diode, where the voltage is less than V_F but greater than $-V_{BR}$. In this mode current flow is mostly blocked,
- **Breakdown:** When the voltage applied across the diode is very large and negative, lots of current will be able to flow in the reverse direction, from cathode to anode

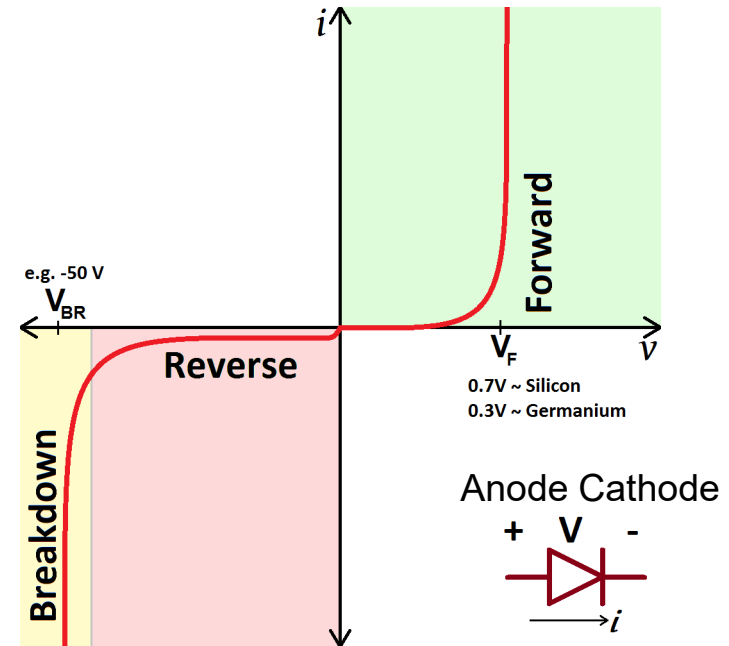

Half-Wave Rectifier

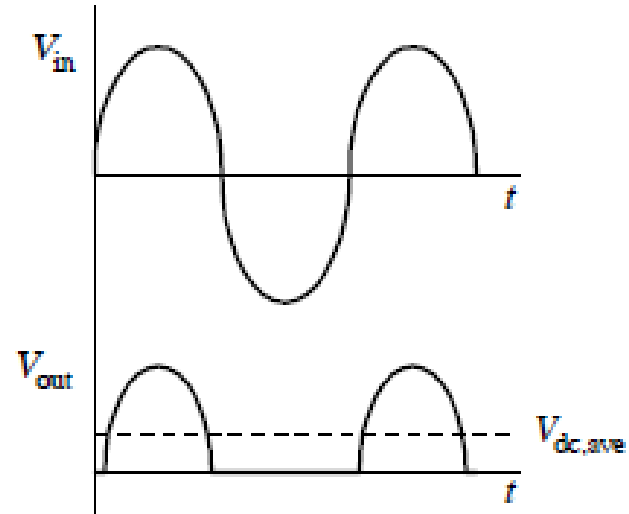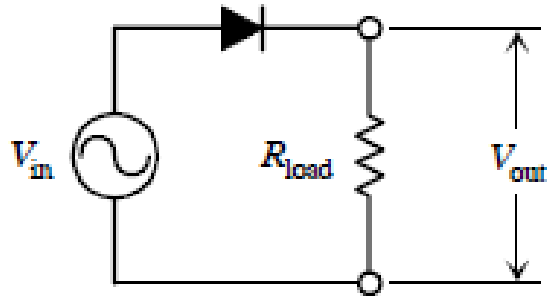

Full-Wave Bridge Rectifier

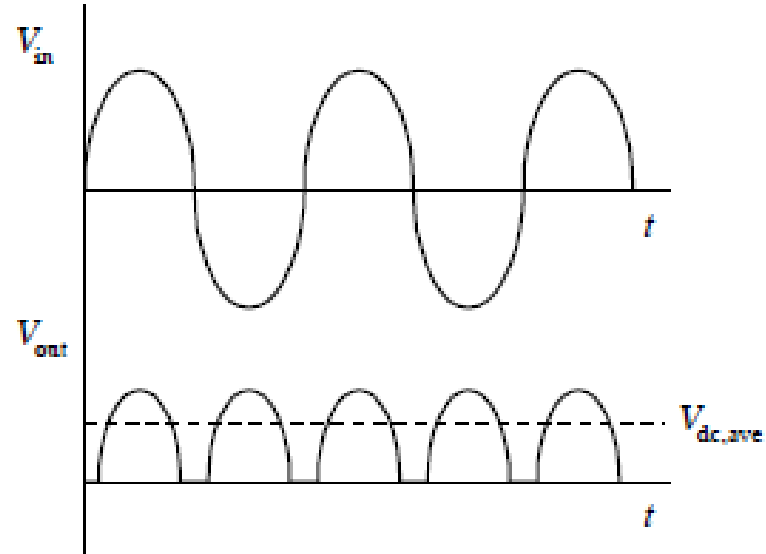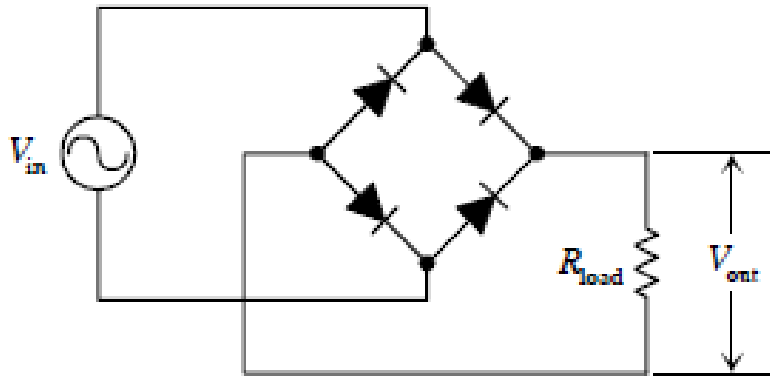



Zener Diode

- A Zener diode is designed to operate in the reverse breakdown, or Zener region, beyond the peak inverse voltage rating of normal diodes.
 - This reverse breakdown voltage is called the Zener test voltage (V_{zt}), which can range between 2.4 V and 200 V.
- In the forward region, it starts conducting around 0.7 V, just like an ordinary silicon diode.
 - In the leakage region, between zero and breakdown, it has only a small reverse current.
 - The breakdown has a sharp knee, followed by an almost vertical increase in current.
- Zener diodes are used primarily for voltage regulation or voltage reference because they maintain constant output voltage despite changes in current.




Zener Diode Voltage Regulator...

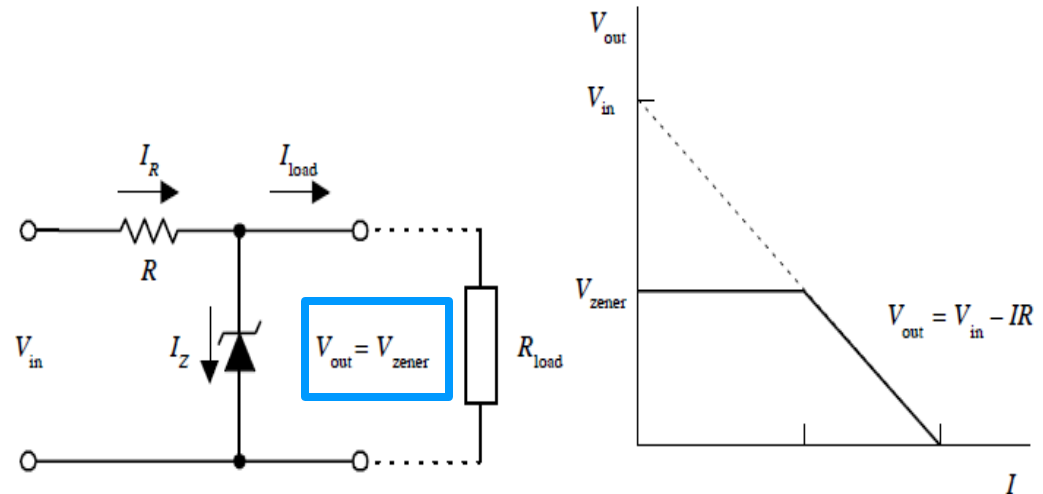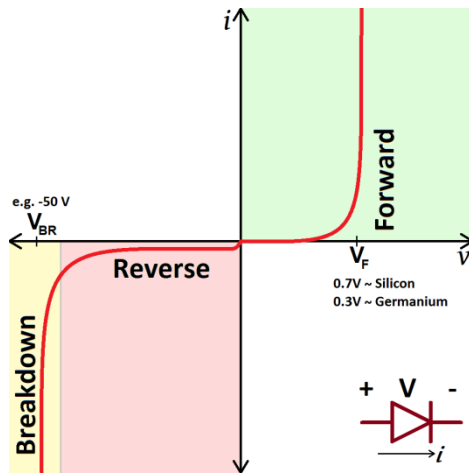1. $I_{load} = \frac{V_{in}}{R_{load}} \approx \frac{V_{Zener}}{R_{load}}$
2. $I_R = \frac{V_{in} - V_{out}}{R} \approx \frac{V_{in} - V_{Zener}}{R}$
3. $I_{Zener} = I_R - I_{load}$




Zener Voltage Regulator Example...


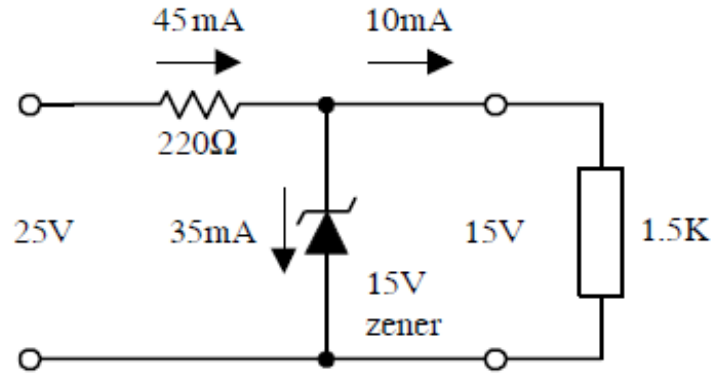


1. $I_{load} = \frac{15V}{1.5k} = 10mA$
2. $I_R = \frac{25V - 15V}{220\Omega} = 45mA$
3. $I_{Zener} = 45mA - 10mA = 35mA$

Zener Diode Simulation...

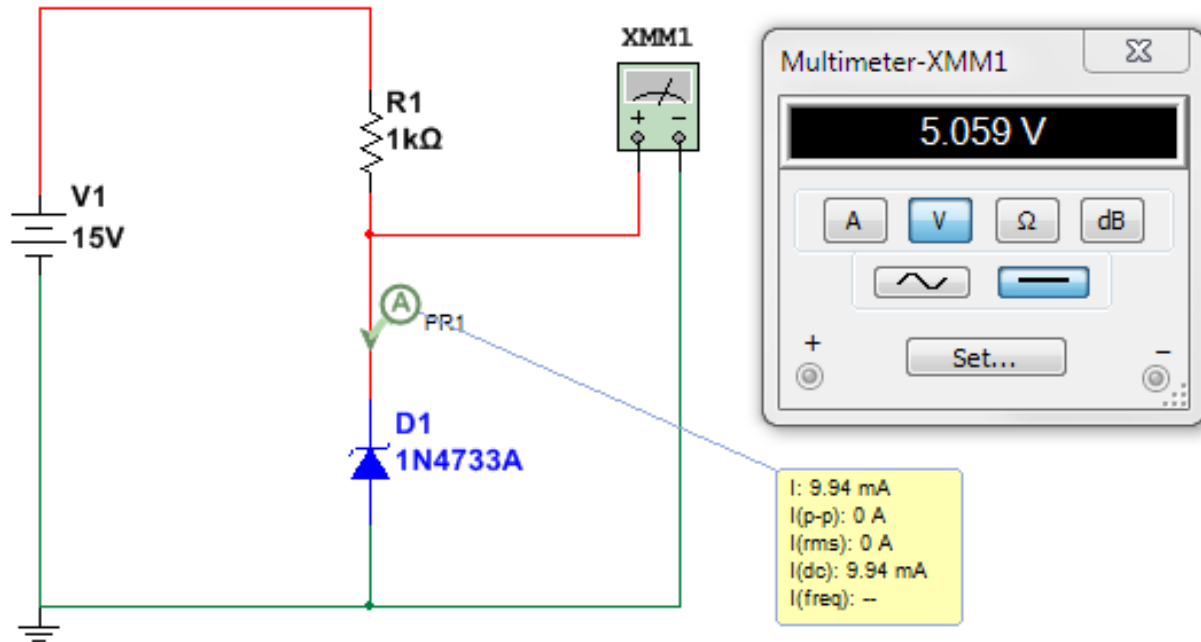



Voltage Regulators – 7800/7900 Series

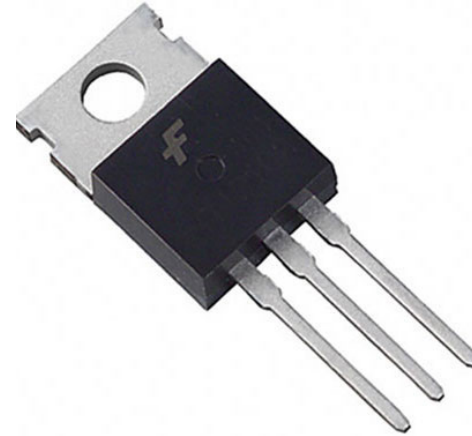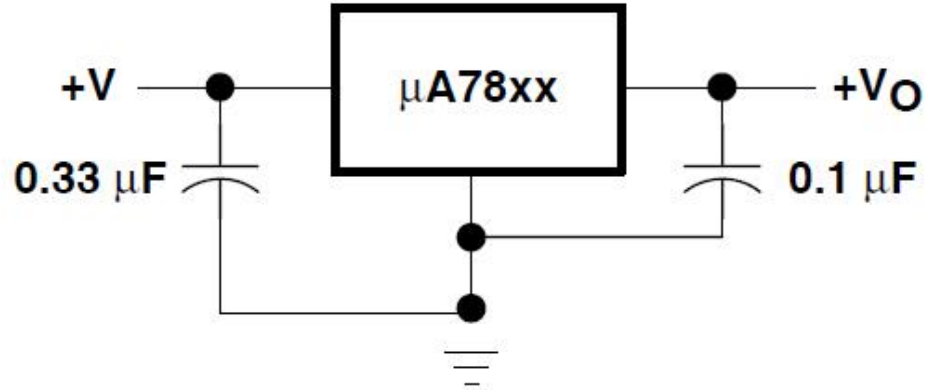

- Fixed voltage integrated voltage regulator.
- Three terminal regulation.
- Output current to 1.5A
- Internal thermal overload protection.
- High-power dissipation capability with heatsink tab.


Transistors

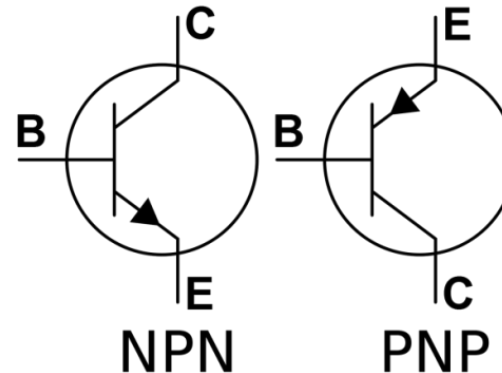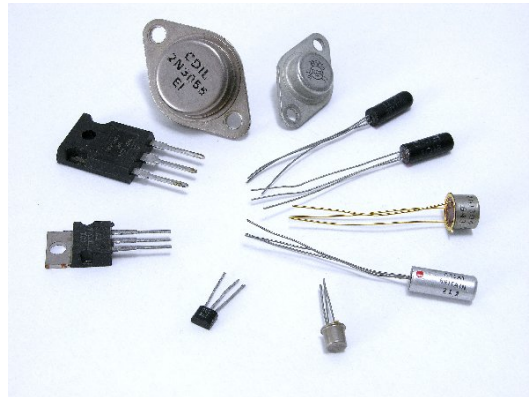- Semiconductor devices that are used to *switch* or *amplify* a signal.
- They typically consist of three terminals. For an NPN or PNP bipolar junction transistor these are called the collector, base and emitter.
- They may be a discrete component, or through nanofabrication may number in the billions for a single CPU – e.g. 7.2 billion in Intel’s 22-core chip.



Transistor as a Switch – On/Off


- Calculations for transistor saturation:
 - With sufficient base current, I_B through R_B , the transistor “switches on” or goes into *saturation*, and *sinks* the load current I_C (turning *off* the V_{out}),
 - When the transistor is off, output current is available through R_C .
 - Calculate the base and collector resistors to allow saturation, and a useful output voltage for this example with the following specifications:
 1. $V_{IN} = 12\text{ V}$, $V_{OUT} < 0.4\text{ V}$ at $I_{SINK} < 10\text{ mA}$ (transistor *on*).
 2. $V_{IN} < 0.05\text{ V}$, $V_{OUT} > 10\text{ V}$ at $I_{OUT} = 1\text{ mA}$ (transistor *off*).
 3. The transistor current gain, β (beta) is 50, and equals I_C/I_B .

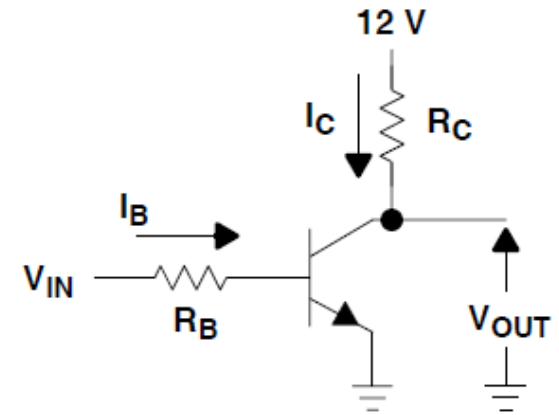

Calculating the Resistors and Current...

- When the transistor is *off*, 1 mA can be drawn out of the collector resistor without pulling the collector or output voltage to less than ten volts (circuit specification) (V_{CE} is voltage from collector to emitter):
 - $R_C \leq \frac{V_{+12} - V_{Out}}{I_{Out}} = \frac{12 - 10}{.001} = 2k$
- When the transistor is *on*, the base resistor must be sized to enable the input signal to drive enough base current into the transistor to saturate it:
 - $I_C = \beta I_B = \frac{V_{+12} - V_{CE}}{R_C} + I_L \approx \frac{V_{+12}}{R_C} + I_L$ (*saturation plus sink current*)
 - $R_B \leq \frac{V_{In} - V_{BE}}{I_B}$ (V_{BE} is voltage from base to emitter)
 - $\therefore R_B \leq \frac{(V_{In} - V_{BE})\beta}{I_C} = \frac{(12 - 0.6)50 V}{\left[\frac{12}{2} + 10\right] mA} = 35.6k$
- When the transistor goes *on*, it sinks the load current.

Transistor Switch Simulation...

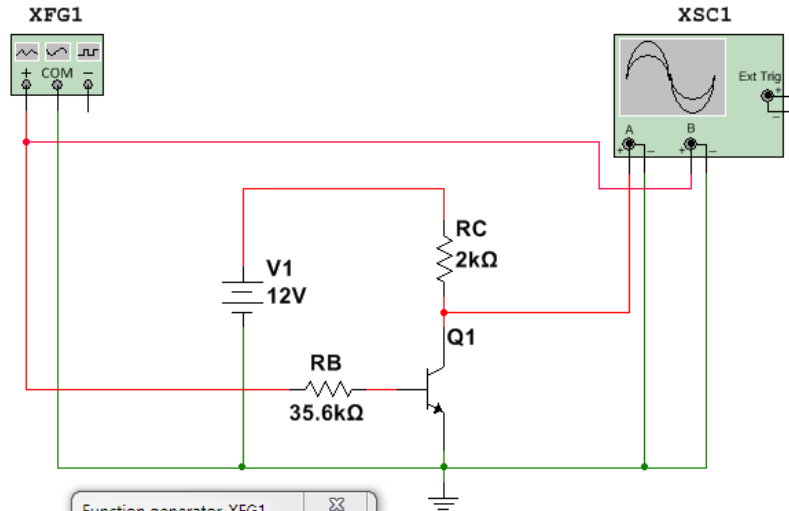

Function generator-XFG1

Waveforms

Signal options

Frequency: 1 Hz


Duty cycle: 50 %

Amplitude: 4 Vp



Offset: 0 V

Set rise/Fall time



Common

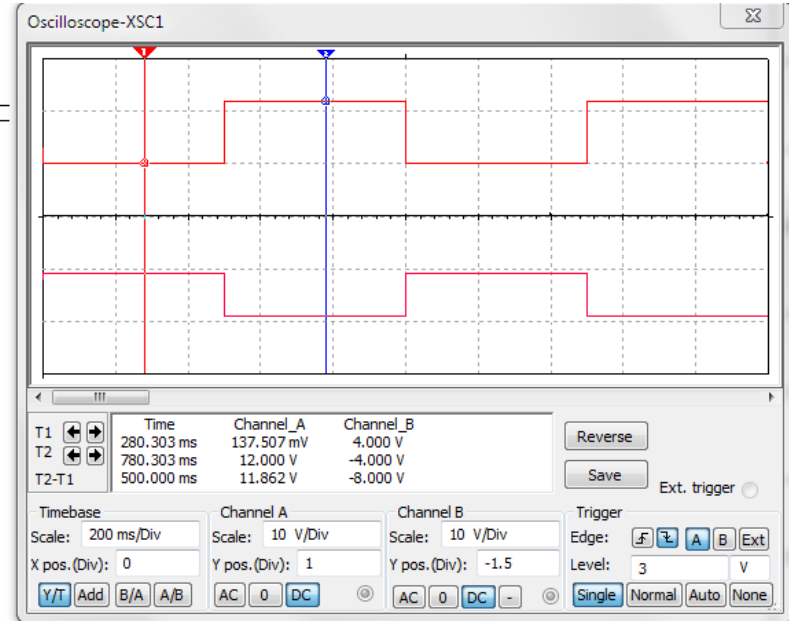

Saturation Voltage...

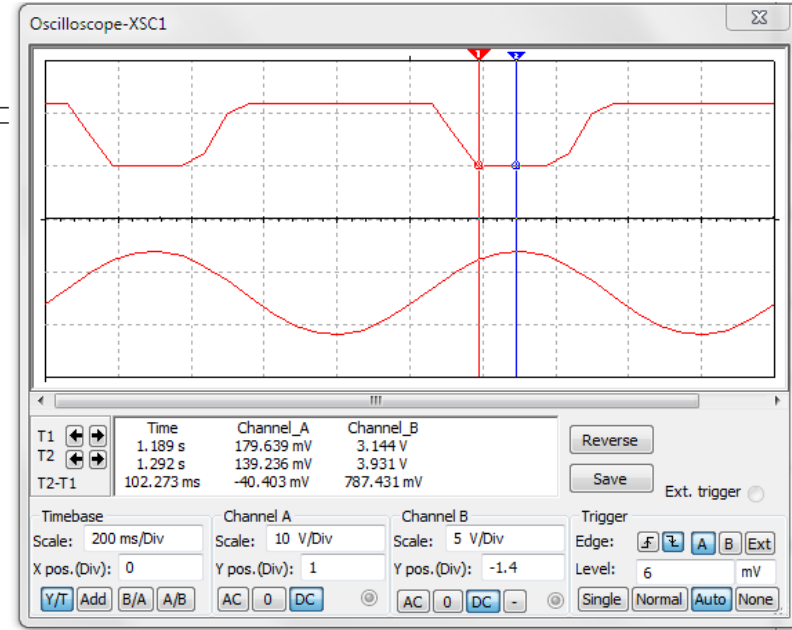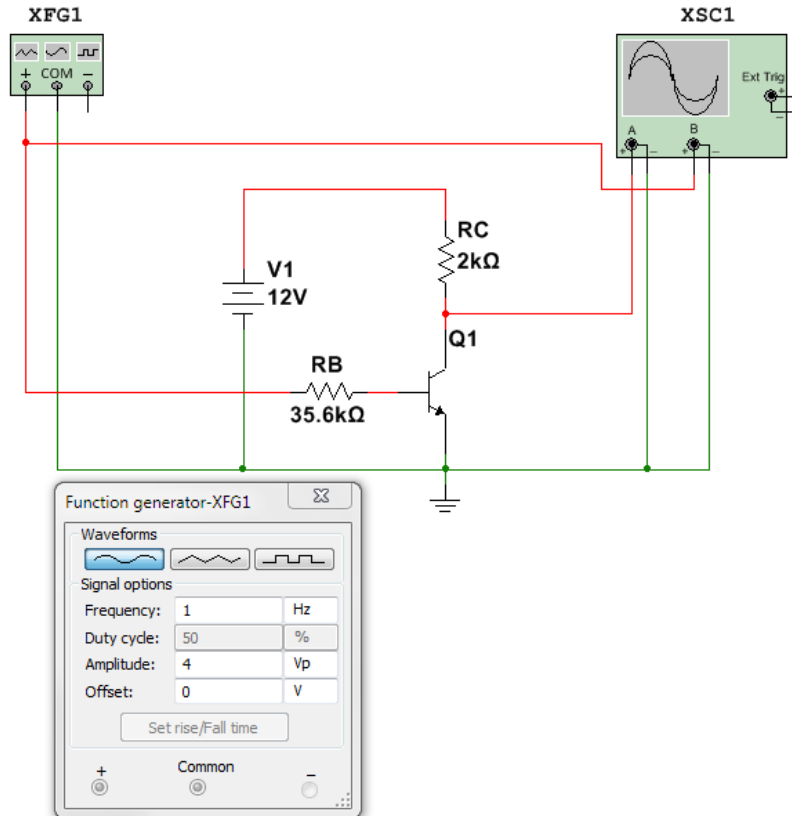

Linear Region...


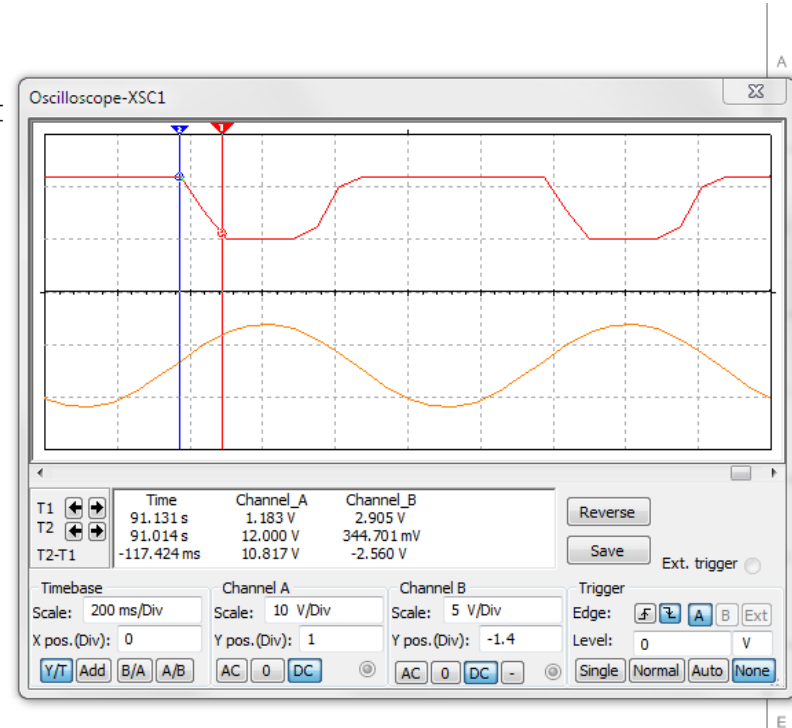
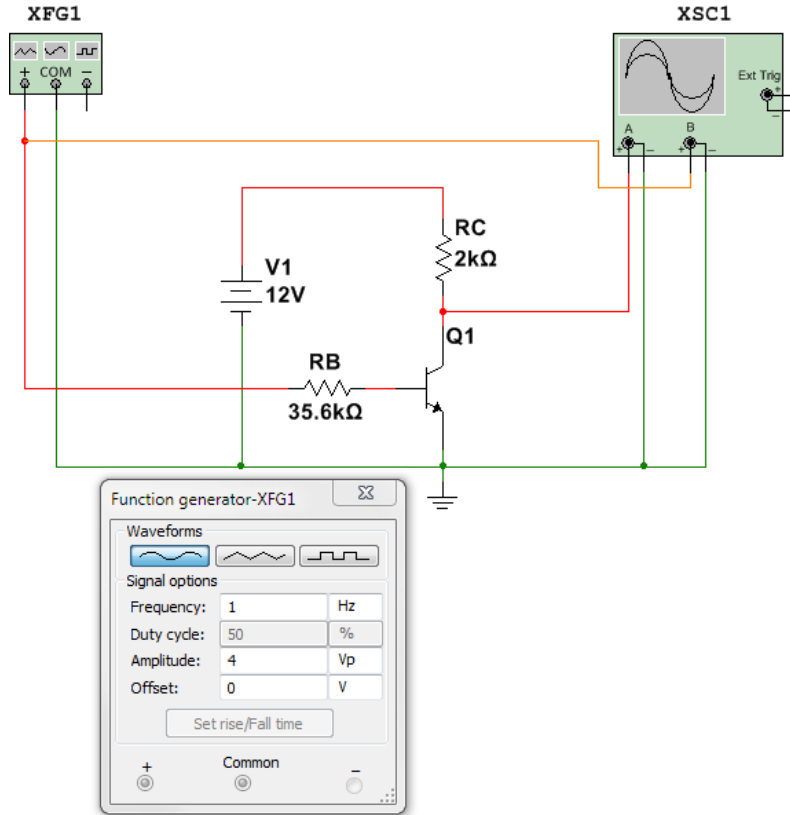


Transistor as an Amplifier

- A transistor can be “off”, “on” or in a “linear state” where I_B causes changes in I_C based on h_{FE} , the current gain factor:
 - $I_C = I_B \times h_{FE}$
 - Useful for example, for a common emitter amplifier.
- In saturation, any changes in I_B will not cause changes in I_C .
- When “off”, there is no base current applied.


Transistor Operating State...

<http://www.ermicro.com/blog>

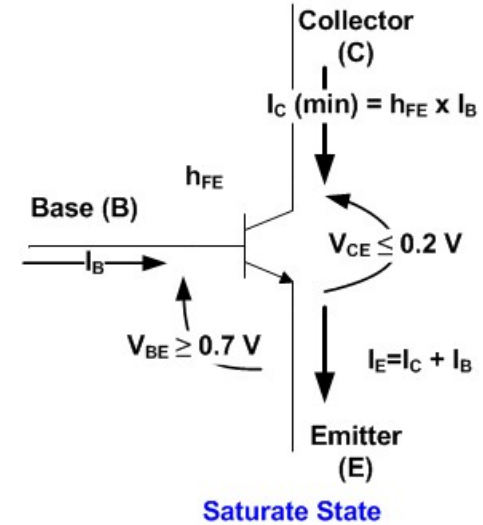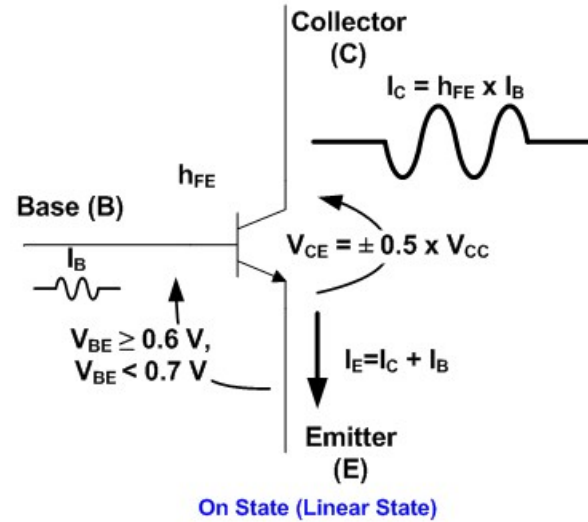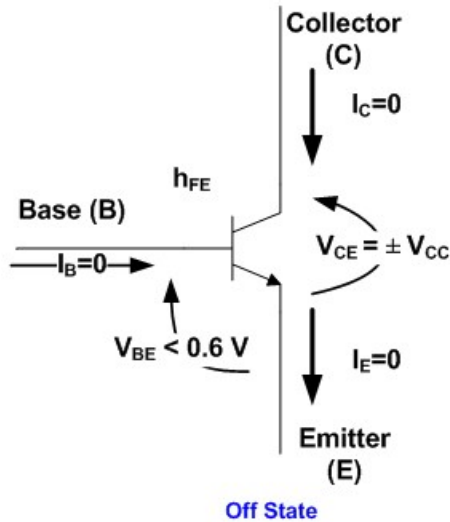

The Transistor Operating State

Typical NPN Characteristic Curve...

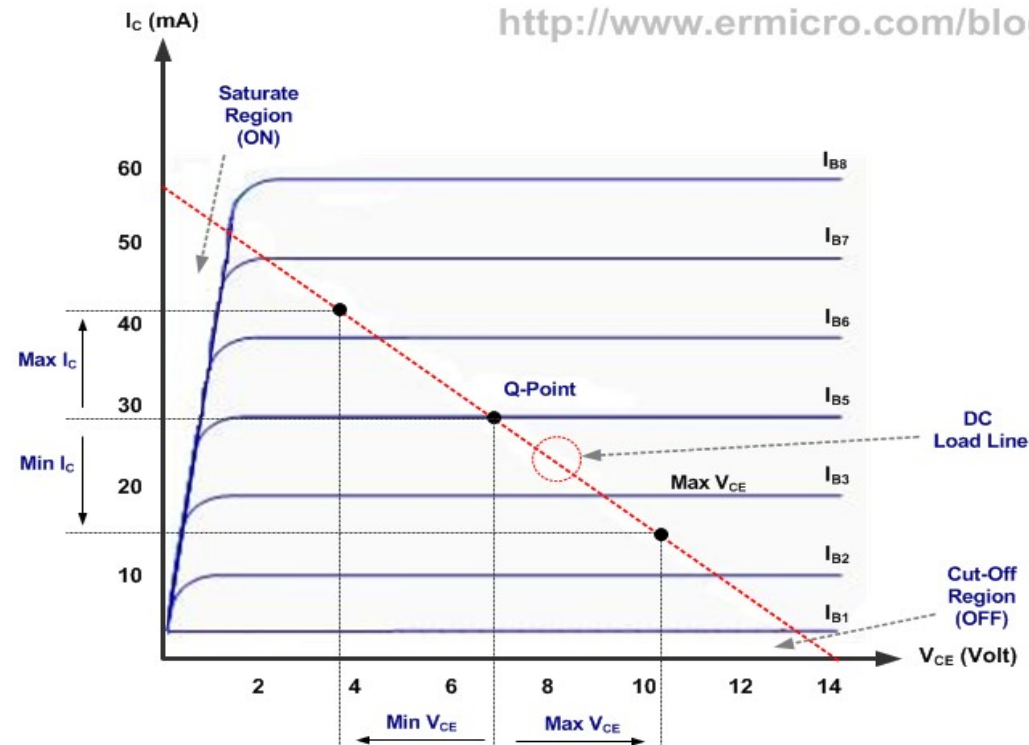

Typical Transistor (NPN) Characteristic Curves for CE (Common Emitter) Amplifier

Curves relate the output collector current, (I_C) to the collector voltage, (V_{CE}) for different values of base current, (I_B).

Quiescent point - V_{CE} is set to allow the output voltage to swing positive and negative when amplifying an AC signal.


Characteristic Curve Explained...

- These curves relate the output collector current, (I_C) to the collector voltage, (V_{CE}) for different values of base current, (I_B).
- A **DC biasing voltage** is applied to the base to allow it to operate in its linear region. The transistor is then operating half-way between its cutoff and saturation voltages.
- The **DC load** line shows all of the possible operating points when different base current values are applied.
- V_{CE} is set to allow the output voltage to swing positive and negative when amplifying an AC signal. This is referred to as setting the operating point or **Quiescent point (Q-point)**.

Bipolar Junction Transistor Amplifier Example ...

● Specifications:

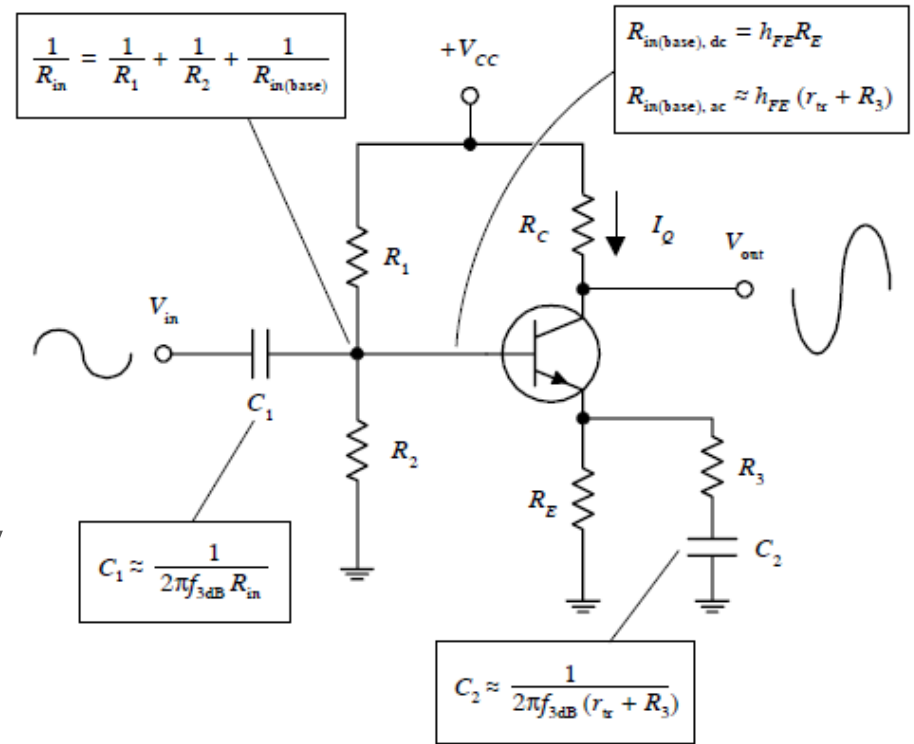1. $I_Q = 1 \text{ mA}$ (I_C)
2. $h_{FE} = 100$ (Gain)
3. $V_{CC} = 20 \text{ V}$ (Source)
4. $f_{3\text{dB}} = 100 \text{ Hz}$
5. V_{BE} is 0.6 V
6. Set V_{OUT} (or V_C) to 10 V
7. Set V_E to 1 V



Common Emitter Amplifier

Calculation of Resistors...

1.
$$R_C = \frac{V_C - V_{CC}}{I_C} = \frac{0.5V_{CC} - V_{CC}}{I_Q} = \frac{10\text{ V}}{1\text{ mA}} = 10\text{ k}\Omega$$

2.
$$R_E = \frac{V_E}{I_E} = \frac{1\text{ V}}{1\text{ mA}} = 1\text{ k}\Omega$$

3.
$$V_B = V_E + 0.6\text{ V} = 1.6\text{ V}$$


4.
$$\frac{R_2}{R_1} = \frac{V_B}{V_{CC} - V_B} = \frac{1.6\text{ V}}{20\text{ V} - 1.6\text{ V}} = \frac{1}{11.5}, R_1 = 11.5R_2$$

5.
$$\frac{R_1 R_2}{R_1 + R_2} \leq \frac{1}{10} R_{in(base),dc}, R_{in(base),dc} = h_{FE} R_E$$

- $R_2 = 10\text{ k}\Omega$
- $R_1 = 115\text{ k}\Omega$ (Substitute $110\text{ k}\Omega$ which exists.)



6. R_3 , C_1 and C_2 are based on gain and frequency.

Simulation of the Amplifier...

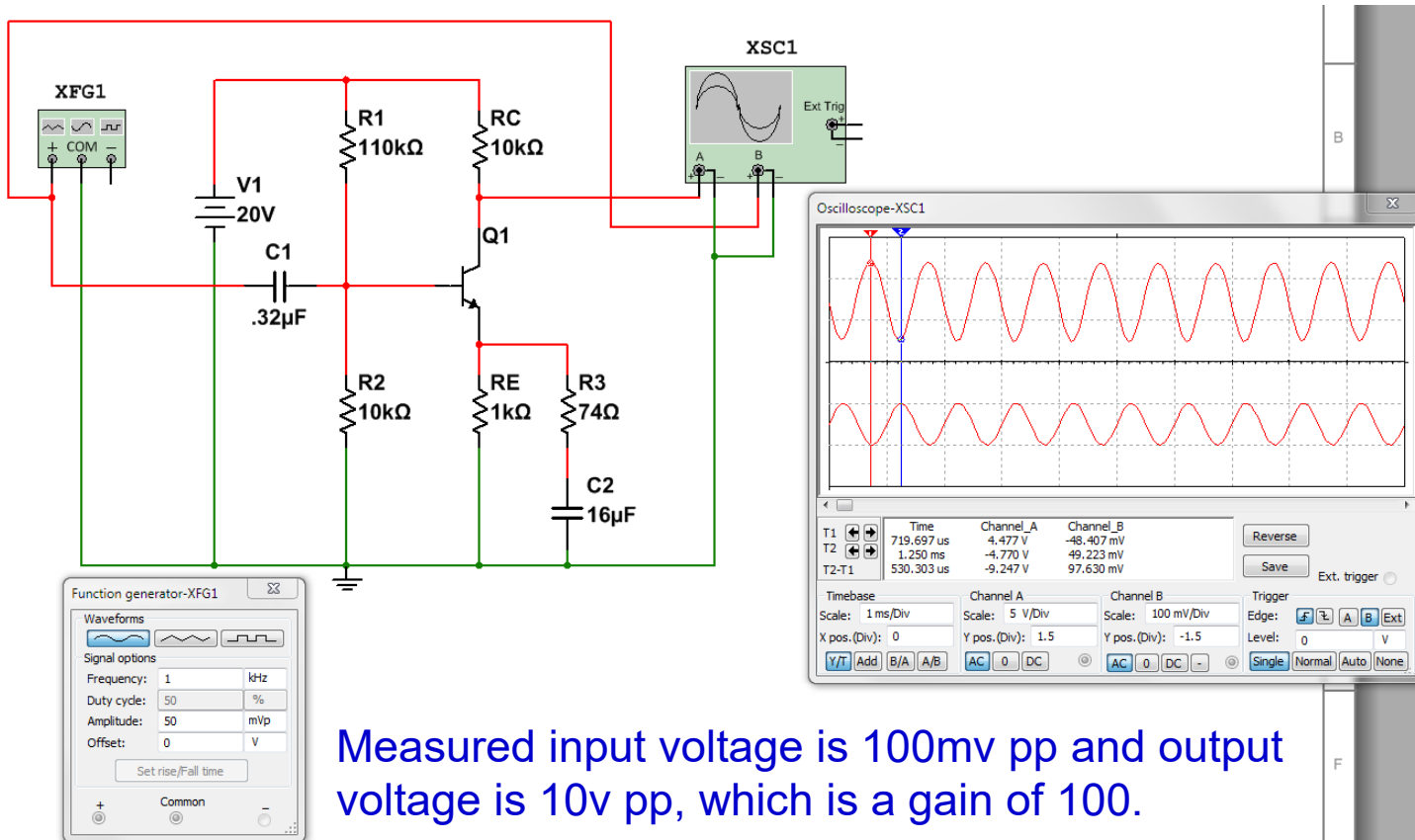

Measured input voltage is 100mv pp and output voltage is 10v pp, which is a gain of 100.

Amplifier on a Breadboard Example...

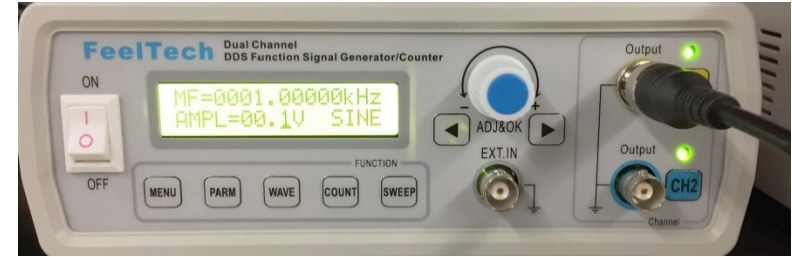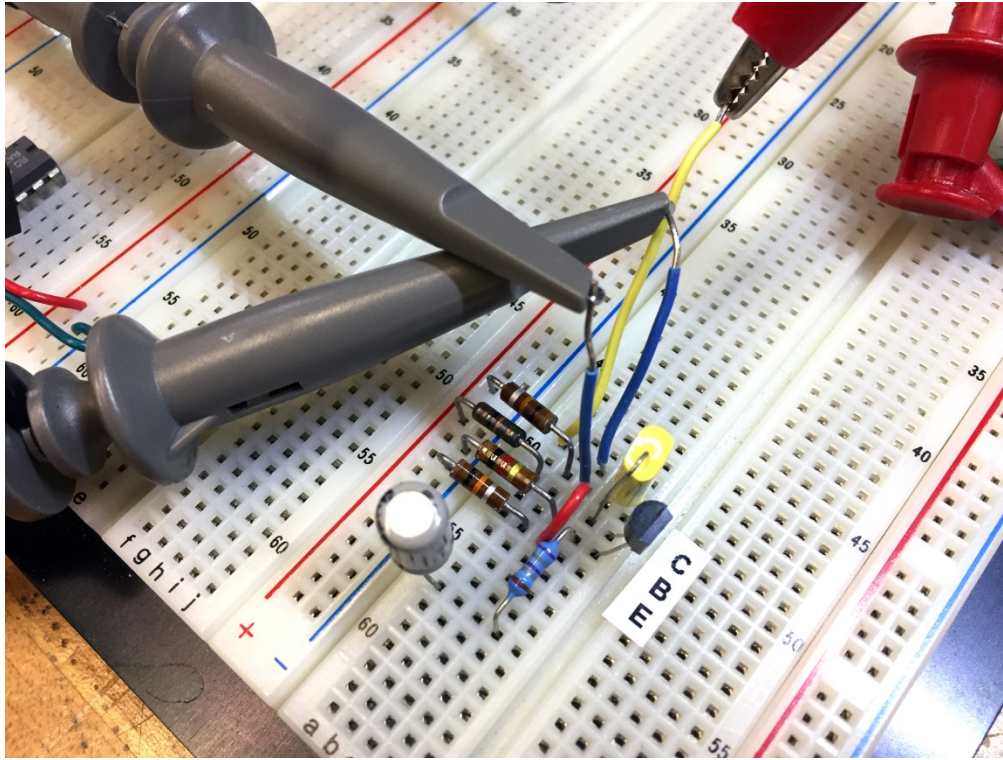


Function Generator set at 1 kHz, 0.1 V pp
(Actually measures 79.2 MV pp on oscilloscope)




Power Supply set at 20 VDC

Voltage Gain...


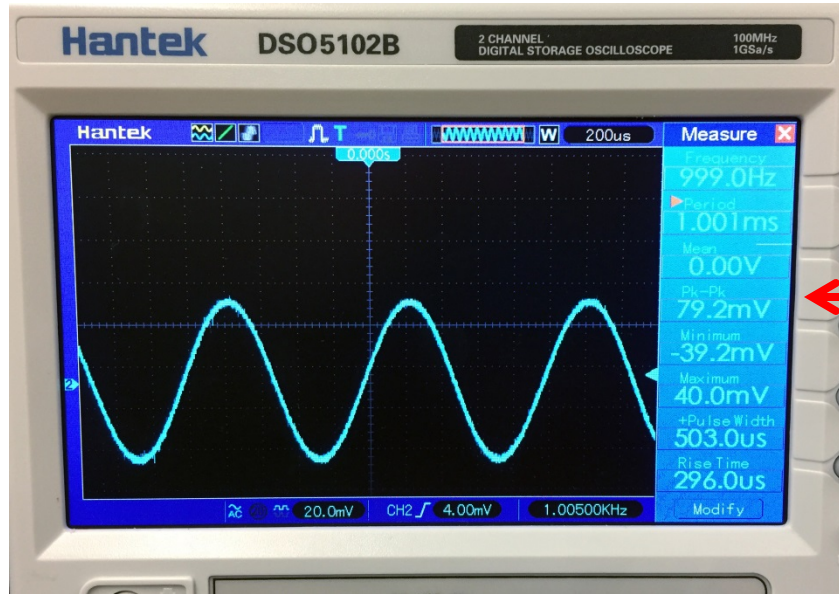


Amplifier Input 79.2 mV pp

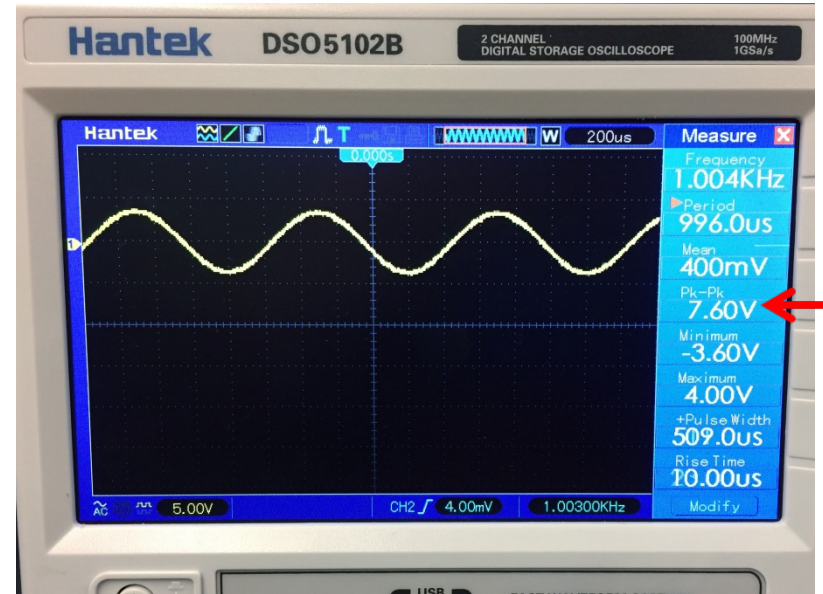

Amplifier Output 7.6 V pp
Gain is $7.6 / .079 = 96.2$

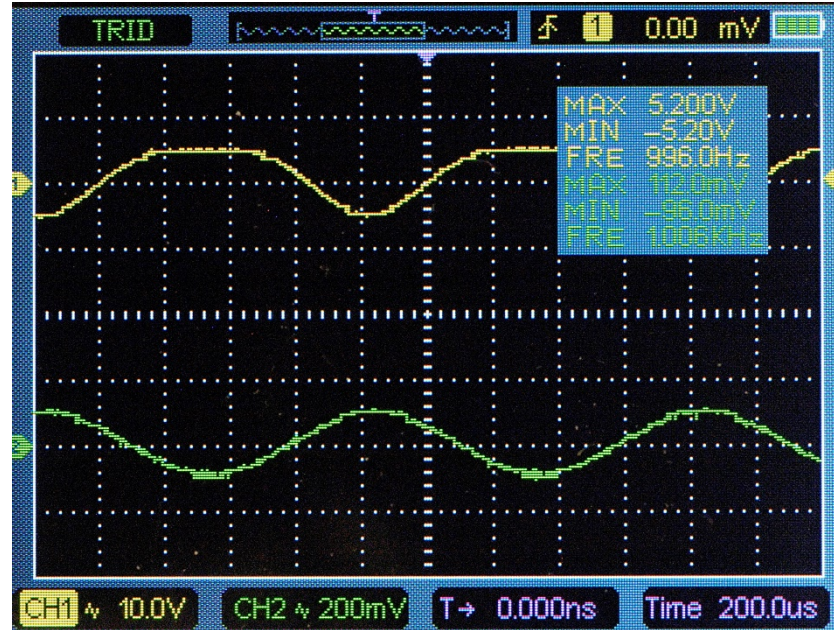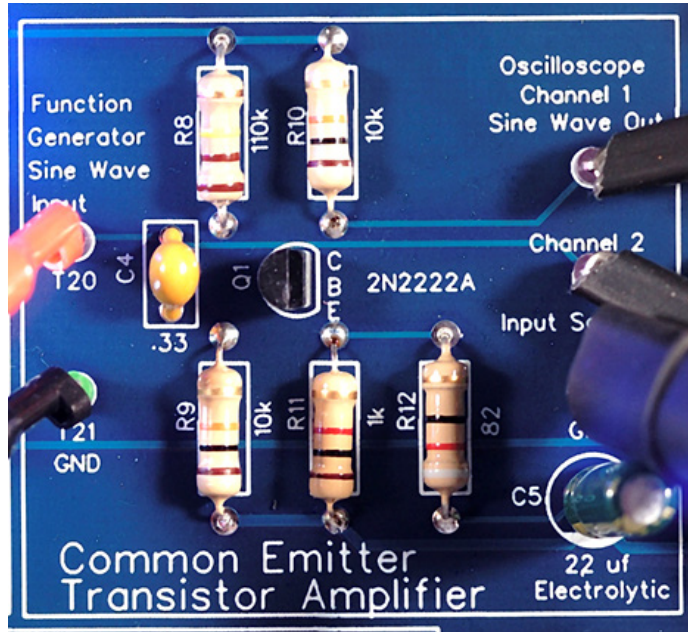Amplifier with the Trainer Board & Hantek 2D72...



- In this example, the input voltage measures 208 mVpp (.112 + .096), and the output voltage measures 10.4 Vpp (5.2 + 5.2).
- The gain is $10.4 / .208 = 50$

Summary

- Semiconductors
 - Diodes to Rectify Current
 - Zener Diodes for Voltage Reference
 - Voltage Regulators
 - Transistors as Switches
 - Common Emitter Transistor Amplifier