 




HOW TO CONTROL DC MOTORS ON AN ARDUINO WITH A TIP120

Posted by Clyde Cox | Arduino | 0



The Arduino's GPIO pins are only capable of delivering a maximum current of 40 mA. Since even small 5V DC motors can draw 50 mA of current or more, it's not recommended to drive DC motors directly from the Arduino's GPIO pins. In this tutorial, we will discuss and learn about the following:

PCBWay HIGH-QUALITY PCB PCB ASSEMBLY
 Free shipping + Free stencil
ONLY \$5 FOR 10 PIECES **ONLY \$30**

- Rogers, HDI, aluminum and rigid-flex PCB are available now
- Production time 24 hours
- Component sourcing
- Quality assurance

- Common issues in connecting and controlling a DC motor requiring high current

FOLLOW US



SUBSCRIBE

Get new tutorials sent to your inbox!

EMAIL ADDRESS

SUBSCRIBE

Circuit Basics
 ULTIMATE GUIDE TO THE ARDUINO VIDEO COURSE
 LEARN MORE


- How a Darlington transistor can be used to drive motors, relays, and solenoids with the Arduino
- How to control the speed of a DC motor using the TIP120 Darlington transistor and an Arduino

BONUS: I made a quick start guide for this tutorial that you can [download](#) and go back to later if you can't set this up right now. It covers all of the steps, diagrams, and code you need to get started.

WHAT'S THE PROBLEM WITH INDUCTIVE LOADS?

Current flowing through a conductor creates a magnetic field around it. By wrapping the wire around an iron bar, you can create a rather strong electromagnet. DC motors have an internal permanent magnet with a coil of wire suspended inside the magnetic field of the permanent magnet. The coil, when energized, interacts with the permanent magnet causing it to spin. As the coil spins, its current stops then reverses direction through the coil which keeps it spinning. Every time current stops flowing through the coil, the electromagnetic field around the coil collapses back into the coils' winding. The collapsing magnetic field induces a current flow in the opposite direction of the original current flow. This is referred to as *back EMF*. Back EMF needs to be addressed since the reverse current can damage the driving device.

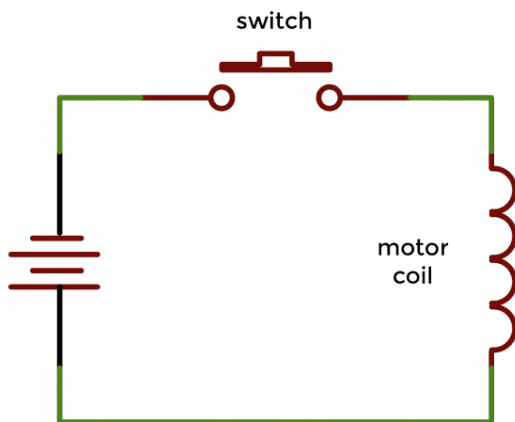With the switch in the open position, no current flows through the coil:



PCBWay

HIGH-QUALITY PCB
ONLY \$5
FOR 10 PIECES

- Rogers, HDI, aluminum and rigid-flex PCB are available now
- Production time 24 hours

PCB ASSEMBLY
Free shipping + Free stencil
ONLY \$30

Component sourcing
Quality assurance

COMPLEX PCB CHOOSE
PCBONLINE

www.pcbonline.com

JLCPCB

Keep Production Even CNY Holidays

\$2 For 5pcs 2Layer PCB

ourPCB

One-Stop Service For PCB&PCBA
2-32 Layers PCB Manufacturing
Turn-Key PCB Assembly
Quick Turn Prototype






Waterford Lismore Double Ol...

WATERFORD

Waterford Lismore Double Old Fashioned Glass | Set of 6 | Crystal

 Closing the switch causes current to flow through the coil setting up a magnetic field (shown in blue) around the coil:



Waterford Marquis Brady Dou...


WATERFORD



Waterford Marquis Brady Double Old Fashioned Glass | Set of 4 | Crystalline




 As soon as the switch is opened again, the magnetic field begins to collapse back into the coils. When a magnetic field cuts through a conductor, it induces a current in the opposite direction.



It's this reverse current that can damage other devices connected to the same circuit.

 However, a diode placed across the motor windings will cause the reverse current to bypass the motor, helping to prevent back EMF.




USING A TIP120 DARLINGTON TRANSISTOR TO DRIVE A DC MOTOR

 
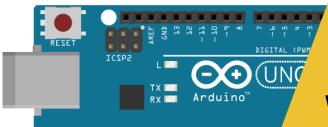
A Darlington transistor is mainly used to provide a very high current gain with a low base current.

HOW DOES THE TIP120 WORK?

The TIP120 is a popular Darlington transistor because it's low-cost, controls voltages up to 60V, and has a high voltage gain. The TIP120 has 2 NPN transistors and a large diode to prevent back EMF. Here's a schematic of the internal circuitry of the TIP120:



Here's a pin diagram for the TIP120:

ULTIMATE GUIDE
TO THE
ARDUINO
VIDEO COURSE

[LEARN MORE](#)




HOW TO CONNECT A DC MOTOR AND TIP120 TO THE ARDUINO

Let's demonstrate how to use the TIP120 on the Arduino by building an example project that controls the speed of a DC motor with a potentiometer. To build this example project, you'll need the following parts:


- [Arduino Pro-Mini](#), or [Arduino Uno](#)
- [TIP120 Darlington transistor](#)
- [DC motor \(5-9 Volts\)](#)
- [2.2K resistor](#)
- [330Ω resistor](#)
- [LED](#)
- [10K potentiometer](#)
- [9V battery](#)
- [Jumper wires](#)
- [Small breadboard](#)

 Follow this wiring diagram to connect the DC motor and TIP120 to the Arduino:



Note that the Arduino is powered by its own 3V power supply, while the DC motor is powered by a separate 9V battery.

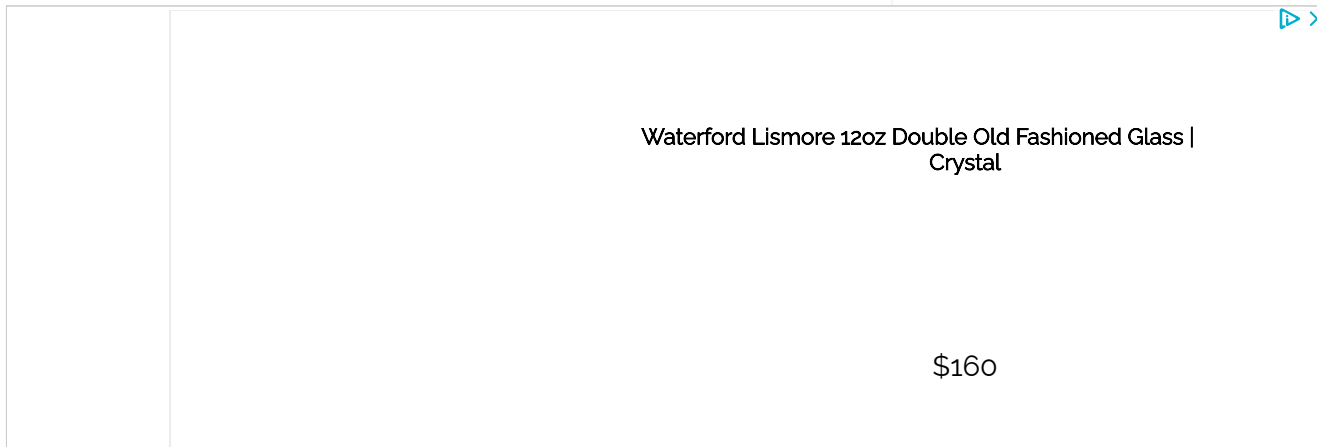If you need help getting started with the Arduino, check out our [Ultimate Guide to the Arduino](#) video course.



HOW TO PROGRAM THE DC MOTOR AND TIP120 ON THE ARDUINO

	Waterford Rose Gold Shamrock Pendant with Stone Disc Set ...	33% OFF	Waterford Times Square Snowglobe	Waterford Lismore 12oz Double Old Fashioned Glass Crystal
	\$150		\$43.55	
	Shop Now		Shop Now	SI
	Waterford Clock Face Insert, Small Round, Roman Numerals		Waterford Lismore 12oz Double Old Fashioned Glass..	W Mar Dc Fashi
	\$15		\$160	
	Shop Now		Shop Now	SI

After you've connected all of the parts as shown in the wiring diagram above, you're ready to program the Arduino. Upload this code to the Arduino:

[1. Electrical Engineering](#)

[6. AC Step Down](#)

[2. High Power Amplifiers](#)

[7. Cheap Industrial](#)

[3. PCB Layout](#)

[8. Wireless Temperature](#)

[4. Free Python Tutorials](#)

[9. New Hi-Tech Gadgets](#)

[5. Easy Data Visualization](#)

[10. PCB Manufacturing](#)

```
int speedSet = A0;
int Tip120 = 11;
int speedVal = 0;
int motorSpeed = 0;
```

```

int motorLimit = 0;
int LED = 9;

void setup() {
  pinMode(LED, OUTPUT);
  Serial.begin(9600);
}

void loop() {
  speedVal = analogRead(speedSet);
  motorSpeed = map(speedVal, 0, 1023, 0, 255);
  if (motorSpeed <= motorLimit)
  {
    digitalWrite(Tip120, LOW);
    digitalWrite(LED, HIGH);
  }
  else
  {
    digitalWrite(LED, LOW);
    analogWrite(Tip120, motorSpeed);
  }
  Serial.print("motorSpeed = " );
  Serial.print(motorSpeed);
  Serial.print(" motorLimit = ");
  Serial.println(motorLimit);
  delay(5);
}

```

EXPLANATION OF THE CODE


DC motors will run at voltages less than the rated voltage, but they will run inefficiently and can damage the motor. Therefore, we have added an indicator LED that will light up when the voltage is too low to power the motor. The value of `motorLimit` is initially set to zero.

After you upload the sketch above, open up the serial monitor and look at the `motorSpeed` value. This represents the power being sent to the motor. It will be a number between 0 and 255. Adjust the potentiometer until the motor is running smoothly (without any buzzing) and write down the `motorSpeed` value.

	Waterford Marquis Brady Double Old Fashioned G...	Waterford Lismore Connoisseur Heritage Ro...	Waterford Diamond Line Double Old Fashioned G...	Waterford Diamond Encr
	\$50	\$325	\$135	\$29
	Shop Now	Shop Now	Shop Now	Shop Now

Now go back to the sketch and set the `motorLimit` variable equal to a number slightly greater than the `motorSpeed` value you wrote down. Then upload the sketch again, and you should see that the

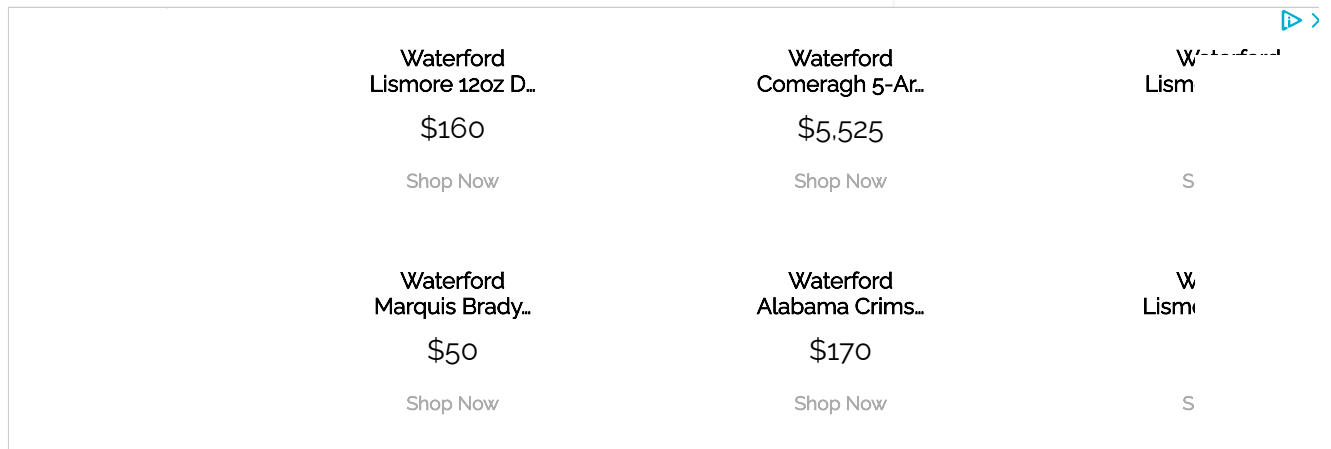motor shuts off when the power is too low. The LED will also light up, indicating that the motor is off. This prevents the motor from starting until there is enough power for it to run properly.



If the motor is running too fast, create a high-speed cut-off by adding the variable `int motorMax = xxx` to the sketch above. Set `xxx` to whatever upper limit is necessary, up to 255. Then, on the line where it says `if (motorSpeed <= motorLimit)`, change it to `if (motorSpeed <= motorLimit || motorSpeed >= motorMax)`. The program will now cut off the motor at the lower and upper limits.

The sketch above uses the following variables:

- `speedSet` is set equal to the analog pin (A0) that takes the input from the potentiometer
- `Tip120` is set equal to the output pin that connects to the TIP120 transistor
- `speedVal` is used to store the value returned by the `analogRead()` function
- `motorSpeed` is set equal to a number between 0 and 255, which will be passed to the `analogWrite()` function to drive the motor
- `motorLimit` is set equal to a cutoff value that will be used to turn off the motor at slow speeds
- `LED` is set equal to the pin connected to the indicator LED

In the sketch above, the variable `speedVal` will contain an integer from 0 to 1023, depending on the value output by the `analogRead()` function. It takes the analog voltage applied to `speedSet` (analog pin A0) and converts it into an integer stored in `speedVal`. In the next line, the `map()` function takes the value stored in `speedVal` and converts it to a value between 0 and 255. The mapped value is stored in the `motorSpeed` variable. The `motorSpeed` variable is passed to the `analogWrite()` function later

in the code to create a pulse width modulation (PWM) signal that is sent to the Tip120 pin.

The if statement performs a comparison to see if the `motorSpeed` variable is less than the `motorLimit` variable. If `motorSpeed` is less than `motorLimit`, `Tip120` is set to LOW, turning off the motor and turning ON the LED indicator. Otherwise, the command `analogWrite(Tip120, motorSpeed)` sends the PWM signal to drive the motor with `analogWrite(Tip120, motorSpeed);`.



JLCPCB - Only \$2 for PCB Prototype (Any Color)
Great Quality Approved by 600,000+ Customers,
10,000+ PCB Orders Per Day.

Sign Up & Get at Least Two \$5 Coupons

Now: <https://jlcpcb.com/quote>


Circuit Basics

ULTIMATE GUIDE
TO THE
ARDUINO
VIDEO COURSE


LEARN MORE

SHARE:     


RELATED POSTS

 

How to Write

 

How to Set up

 

Make an

Turn Any Appliance into a Smart Device with an Arduino Controlled Power Outlet

Arduino Data to Files on an SD Card

Seven Segment Displays on the Arduino

Arduino Temperature Sensor (Thermistor Tutorial)

1. New Hi-	6. Wireless
2. Three	7. PCB
3. Easy Data	8. Free
4. LCD Touch	9. AC Step
5. Distance	10. High

Four vertical input fields with colored borders: blue, blue, orange, and green.

LEAVE A REPLY

Your email address will not be published. Required fields are marked *

COMMENT

NAME *

EMAIL *

WEBSITE

Save my name, email, and website in this browser for the next time I comment.

Notify me of follow-up comments by email.

Notify me of new posts by email.

For security, use of Google's reCAPTCHA service is required which is subject to the Google [Privacy Policy](#) and [Terms of Use](#).

[I agree to these terms.](#)

POST COMMENT

Copyright **Circuit Basics**

[Raspberry Pi](#) [Arduino](#) [DIY Electronics](#) [Programming](#) [Videos](#) [Resources](#) [About](#) [Contact Us](#) [Privacy Policy](#)

